

```
1  `timescale 1ns / 1ps
2  /*****
3   * File Name: hex_to_7seg.v
4   * Project: Counter using AISO
5   * Designer: Marc Cabote
6   * Email: marcdominic011@gmail.com
7   * Rev. Date: 20 September 2017
8   *
9   * Purpose: The Hex-to-7-Segment module is a combinational logic circuit designed
10  *           to convert a 4-bit hexadecimal input value into a 7-bit 7-segment output.
11  *           The various cathodes represent the seven segments of a single anode on the
12  *           Nexys4 DDR 7-segment display. If a cathode is set to 1'b0, its
13  *           corresponding
14  *           segment will turn on. If a cathode is set to 1'b1, its corresponding
15  *           segment
16  *           will turn off.
17  *
18  * Notes:   - Each segment in the LED 7-segment diplay is represented by letters a-g.
19  *           - A segment will turn on if its cathode has a lower value than its anode.
20  *           *****/
21 module hex_to_7seg(input      [3:0] hex,
22                   output reg  a, b, c, d, e, f, g
23                   );
24
25     // Execute block if hex changes
26     always @( hex ) begin
27         case( hex )
28             4'b0000: {a, b, c, d, e, f, g} = 7'b0000001; // 7-segment code for 0
29             4'b0001: {a, b, c, d, e, f, g} = 7'b1001111; // 7-segment code for 1
30             4'b0010: {a, b, c, d, e, f, g} = 7'b0010010; // 7-segment code for 2
31             4'b0011: {a, b, c, d, e, f, g} = 7'b0000110; // 7-segment code for 3
32             4'b0100: {a, b, c, d, e, f, g} = 7'b1001100; // 7-segment code for 4
33             4'b0101: {a, b, c, d, e, f, g} = 7'b0100100; // 7-segment code for 5
34             4'b0110: {a, b, c, d, e, f, g} = 7'b0100000; // 7-segment code for 6
35             4'b0111: {a, b, c, d, e, f, g} = 7'b0001111; // 7-segment code for 7
36             4'b1000: {a, b, c, d, e, f, g} = 7'b0000000; // 7-segment code for 8
37             4'b1001: {a, b, c, d, e, f, g} = 7'b0000100; // 7-segment code for 9
38             4'b1010: {a, b, c, d, e, f, g} = 7'b0001000; // 7-segment code for A
39             4'b1011: {a, b, c, d, e, f, g} = 7'b1100000; // 7-segment code for B
40             4'b1100: {a, b, c, d, e, f, g} = 7'b0110001; // 7-segment code for C
41             4'b1101: {a, b, c, d, e, f, g} = 7'b1000010; // 7-segment code for D
42             4'b1110: {a, b, c, d, e, f, g} = 7'b0110000; // 7-segment code for E
43             4'b1111: {a, b, c, d, e, f, g} = 7'b0111000; // 7-segment code for F
44             default: {a, b, c, d, e, f, g} = 7'b1111111; // Default Case
45         endcase
46     end
47 endmodule
```